

Computer Organization

(Logic circuits design and minimization)

KR Chowdhary
Professor & Head
Email: kr.chowdhary@gmail.com
webpage: krchowdhary.com

Department of Computer Science and Engineering
MBM Engineering College, Jodhpur

November 14, 2013

- ▶ Instructions and data are in binary (1, 0) format
- ▶ Binary Levels in logics: TTL (0-0.8) = logic 0, (2.0-5.0 v) = logic 1(true). Other are ECL, DTL, RTL, etc.
- ▶ How the CPU identifies a binary string as Data or Instructions?
- ▶ What is Minimum circuit to store a bit (0 / 1)?

Single Memory Cell

- ▶ Flip-flop(Bipolar Transistor) as single memory cell.
- ▶ One transistor is always in saturation and other in cutoff. See figure
- ▶ Why?


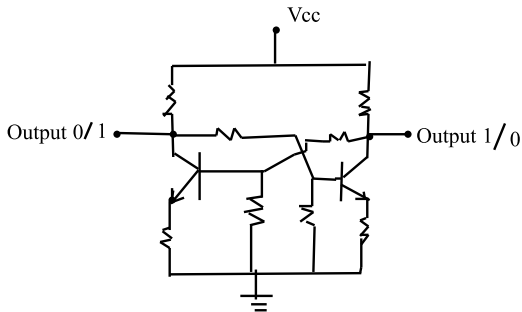



Figure: Single cell to store 1 or 0

▶ basic gates and universal gates

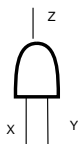


Truth table AND GATE

X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

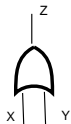


truth Table OR GATE

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

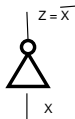


TT not gate

X	Z
0	1
1	0

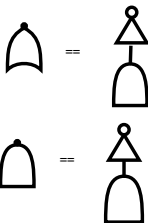


A TTL NAND gate

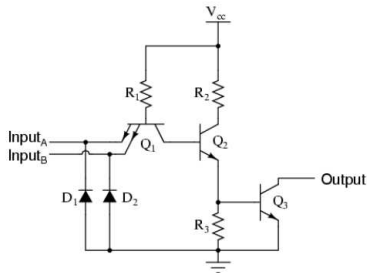

- ▶ **Fan-In:** The maximum number of gates which can be connected input to a gate.
- ▶ **Fan-Out:** The maximum number of gates which can be connected at the output of a gate.

Simple Boolean Logic Circuits

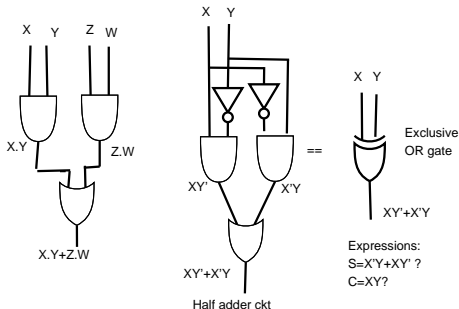- ▶ Building circuits from basic gates
- ▶ These are called **Combinational Circuits** (they have no memory element)
- ▶ **Sequential circuits:** O/P is function of current I/P and previous I/P.




These circuits' output is directly dependent on I/P?

Standard forms of expressions

- ▶ We can write expressions in many ways, but some ways are more useful than others
 - ▶ A **sum of products (SOP) expression** contains:
 - Only OR (sum) operations at the “outermost” level
 - Each term that is summed must be a product of literals
- $$f(x, y, z) = y' + x'yz' + xz$$
- ▶ The advantage is that any sum of products expression can be implemented using a two-level circuit

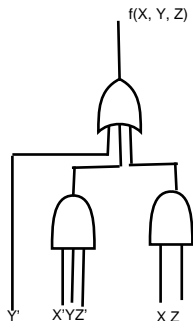- literals and their complements at the “0th” level
- AND gates at the first level
- a single OR gate at the second level



- ▶ A **minterm is a special product of literals**, in which each input variable appears exactly once.
- ▶ A function with n variables has 2^n minterms (since each variable can appear complemented or not)
- ▶ A three-variable function, such as $f(x, y, z)$, has $2^3 = 8$ minterms

$x'y'z', x'y'z, x'yz', x'yz, xy'z', xy'z, xyz', xyz$
($m_0, m_1, m_2, m_3, m_4, m_5, m_6, m_7$ in short)

- ▶ A **product of sums** (POS) expression contains:
 - Only AND (product) operations at the “outermost” level
 - Each term must be a sum of literals
- ▶ Product of sums expressions can be implemented with two-level circuits
 - literals and their complements at the “0th” level
 - OR gates at the first level
 - a single AND gate at the second level

$$f(x, y, z) = y'(x' + y + z')(x + z)$$

- ▶ A **maxterm is a sum of literals**, in which each input variable appears exactly once.
- ▶ A function with n variables has 2^n maxterms
- ▶ Each maxterm is false for exactly one combination of inputs:
- ▶ The maxterms for a three-variable function $f(x,y,z)$:
 $(x' + y' + z') \dots (x + y + z)$ (M_0, \dots, M_7 in short)
Product of maxterms:
- ▶ If you have a truth table for a function, you can write a product of maxterms expression by picking out the rows of the table where the function **output is 0** (Be careful if you are writing the actual literals!)

X	Y	Z	$f(X, Y, Z)$	$f'(X, Y, Z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	1	0
1	1	1	0	1

$$f = (x' + Y + Z)(X' + Y + Z')(X' + Y' + Z')$$

$$= M_4 M_5 M_7$$

$$= \prod M(4, 5, 7)$$

$$f' = (x + Y + Z)(X + Y + Z')(X + Y' + Z)(X + Y' + Z')(X' + Y' + Z)$$

$$= M_0 M_1 M_2 M_3 M_6$$

$$= \prod M(0, 1, 2, 3, 6)$$

Conversion between standard forms


The minterms can be converted into maxterms and vice-versa using De-Morgan's laws. Considering maxterms' expression as

$$\begin{aligned}f' &= \prod M(0, 1, 2, 3, 6) \\ &= M_0 M_1 M_2 M_3 M_6 \\ (f')' &= (M_0 M_1 M_2 M_3 M_6)' \\ f &= (M'_0 + M'_1 + M'_2 + M'_3 + M'_6) \\ &= (m_4 m_5 m_7) \\ &= \sum m(4, 5, 7)\end{aligned}$$

In the similar way, the minterms can be converted into maxterms.



Combinational Circuits

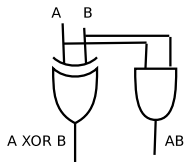- ▶ Adders, Subtractors, Multipliers, Dividers, Multiplexers, Demultiplexers (o/p depends on current input)



truth table

A	B	Sum = $A'B + AB'$ = A XOR B	Carry = AB
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

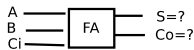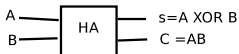

Full Adder (FA) TT:

A	B	Ci	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$S = A \text{ XOR } B \text{ XOR } C_i$
 $Co = AB \text{ OR } AC_i \text{ OR } BC_i$

- ▶ A full adder adds two bits and *carry* of previous addition.
How many FAs are required to add two 4-bit binary numbers?
Why FA is FA?

Max and Min term expressions

$f(x_1, \dots, x_n) = \sum_i x_{i1} \dots x_{in}$, where $x_{ij} = x_{ij} | \overline{x_{ij}}$ (SOP)

$f(x_1, \dots, x_n) = \prod_i (x_{i1} + \dots + x_{in})$. (POS)

The above is called *Quinne-McClusky Method*.

$S = \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i$, from truth table

$C_o = \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$, from truth table

(Or, function $C_o(A, B, C_i) = (m_3, m_5, m_6, m_7)$). The *minterm* m_j assumes a value 1 for unique value of variables. *Maxterm* defines the 0s in the truth table).

Alternatively, sum S is: $(A \oplus B) \oplus C_i$, (\oplus is ex-or)

$$= (\bar{A}B + A\bar{B}) \oplus C_i$$

$$= ABC_i + \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i$$

C_o , the carry out of full adder, is $AB + AC_i + BC_i$

Karnaugh Map for minimization of gate circuits using minterms

After **Maurice Karnaugh** (Bell Labs, 1950)

Karnaugh Map for C_o

	$\bar{B}\bar{C}_i$	$\bar{B}C_i$	BC_i	$B\bar{C}_i$
\bar{A}	0	0	1	0
A	0	1	1	1

$$C_o = AC_i + AB + BC_i$$

The function $C_o(A, B, C_i)$ Can be implemented by three *AND* gates plus one *OR* gate. Alternatively by: four gates each having fan-in 2.

K-map for minimization using maxterms

	$\bar{B}\bar{C}_i$	$\bar{B}C_i$	BC_i	$B\bar{C}_i$
\bar{A}	0	0	1	0
A	0	1	1	1

$$\begin{aligned}C_o(A, B, C_i) &= (A + B)(A + C_i)(B + C_i) \\ &= (A + AC_i + AB + BC_i)(B + C_i) \\ &= \dots \\ &= AB + BC_i + AC_i\end{aligned}$$