

Computer Organization

(Gate Level and Word Level Designs)


KR Chowdhary
Professor & Head
Email: kr.chowdhary@gmail.com
webpage: krchowdhary.com

Department of Computer Science and Engineering
MBM Engineering College, Jodhpur

November 14, 2013


Sequential circuits

Propagation Delay(Δ):

 

$z(t + \Delta) = y(t) = x_1(t) \cdot \bar{x}_2(t)$. The y is internal state variable.

SR Flipflop:

 


Simple SR Flip-flop

- ▶ For $SR=00$, $y_1 = \bar{y}_2 = 0$, or $y_1 = \bar{y}_2 = 1$.
- ▶ For $SR=10$, $y_1 = \bar{y}_2 = 0$.
- ▶ For $SR = 01$, $y_2 = \bar{y}_1 = 0$.


Race Condition:

- ▶ Let $SR = 11$. Thus, $y_1 = y_2 = 0$ after Δ time (i.e., propagation delay). Now let, SR becomes 00 . After delay Δ , $y_1, y_2 = 11$. After further Δ time, $y_1, y_2 = 00$. Then it changes back to 00 , and so on.
- ▶ Thus, output Oscillates between 00 and 11 . For this to happen, $\Delta_1 = \Delta_2$.
- ▶ $SR = 11$ is **forbidden state**. $\Delta_1 \neq \Delta_2$?

Sequential circuits-2

 


 - ▶ Race conditions are eliminated by timing signals (clock)
- ▶ Sequential circuits + clock = Synchronous circuits
- ▶ Circuits **not** timed by clock are asynchronous circuits (Prone to race conditions. Why?)
- ▶ Triggering takes place on rising or trailing edge of clock pulse. Before this, the signals are supposed to be stabilized.




- ▶ Clock active and inactive states: 1, 0. They also correspond to transition from 0-to-1 or 1-to-0.
- ▶ The period, during the time clock is inactive, must be atleast as long as the worst case signal propagation through C , and active period must be long enough to allow M to make one complete transition.
- ▶ Behaviour of seq. ckt is described by [State table](#).
- ▶ What happens if clock period is long and signal passed through forward path feeds back to I/P during true period of CLK?

SR Flip-flop

 

SR Flip-flop Logic diagram

 


SR FF Symbol

- ▶ For $SR=00$, there is no change in output y, \bar{y} .
- ▶ $SR=11$ is forbidden. The $S(\text{set})=1, R(\text{reset})=0$ Sets true o/p y to 1
- ▶ $SR=01$ Resets true o/p y to 0.
- ▶ Let Δ is propagation delay of a gate, and $\tau \approx 2\Delta$.

$$\begin{aligned}y(t+2\Delta) &= \overline{R(t+\Delta) + [S(t) + y(t+\Delta)]} \\ &= \bar{R}(t+\Delta)[S(t) + y(t+\Delta)] \\ y(t+\tau) &\approx \bar{R}(t)[S(t) + y(t)]\end{aligned}$$

Clocked SR Flip-flop



 


SR flip-flop Truth-Table-1


		Input SR		
		00	01	10
current state (y)	0	0	0	1
	1	1	0	1

- ▶ From table-1 above, using minimization, $y(t+1) = \bar{R}(t)[S(t) + y(t)]$, where $y(t+1)$ is new state and $y(t)$ is previous state.
- ▶ Other FFs are derived from SR.
- ▶ No state change occurs without clock pulse
- ▶ The clock pulse should be sufficiently long, to allow the inputs to stabilize
- ▶ P, C inputs are **Preset/Clear** to Set/ Clear without clock

JK and D Flip-flop

   

Logic circuit

 

Symbol

table-2
Input JK

	00	01	10	11
state y	0	0	1	1
1	1	0	1	0

Y = True output, C = Clear signal

- ▶ In JK (derived from SR FF). From table-2, using minimization, $y(t+1) = J(t)\bar{y}(t) + \bar{K}(t)y(t)$
- ▶ for JK=00, there is NO change in output, 10 and 01 causes set and reset of FF, and JK=11 toggles the FF (i.e., I/P 11 is not forbidden).
- ▶ D (Delay)FF has single input only. With $D = 1$, it sets, and with $D = 0$ it resets the FF. $y(t+1) = D(t)$

Gated D-Latch

- ▶ Most commonly used FF are D-FF because they are useful for temporary storage of data
- ▶ SR input will always be 01/10 only. 00/11 input are non-existent, and undefined.
- ▶ During the positive half of clock, D should be stable. Else transition will occur at Q .

 


Figure 1: D-flipflop.

T-Flip-flop

- ▶ A T-FF changes its state every clock cycle(toggles) if its input T is equal to 1.
- ▶ The triggering (level change at o/p) takes place at positive of CLK.

 


Figure 2: T-Flip-flop.

Registers and Shift Registers

- ▶ Registers store machine words. Shift and rotate data.
- ▶ below given circuit is shift-right register.

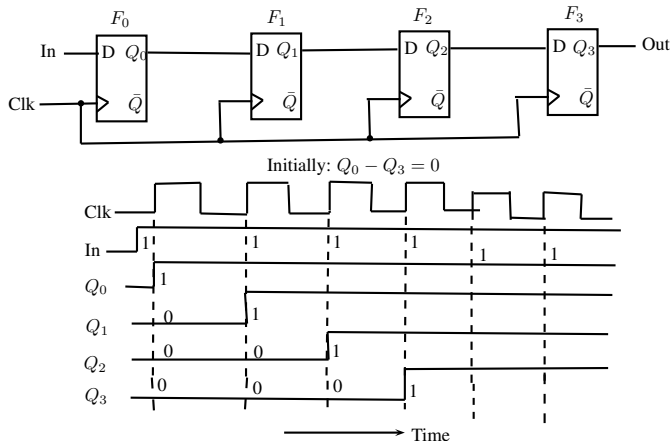


Figure 3: Shift-right register.

Parallel Shift Registers

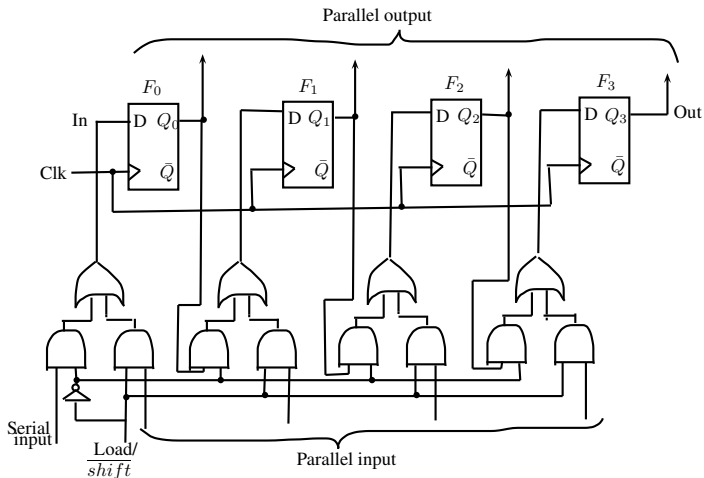


Figure 4: Parallel Shift register.

4-bit up-counter


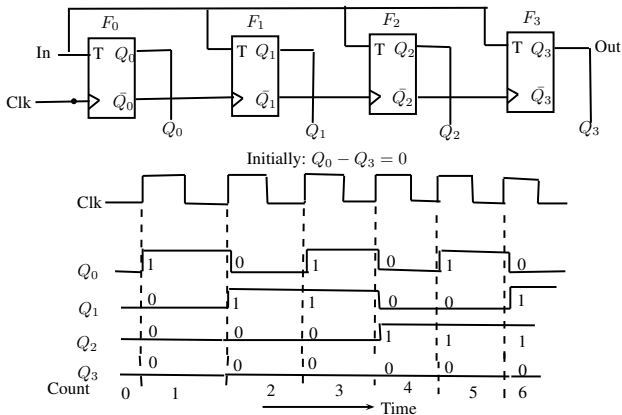


Figure 5: Asynchronous counter.

 - ▶ Counters generate control and timing signals
- ▶ Q_0 freq. = $clk/2$, q_1 fre. = $clk/4$, ..., called **ripple counter**.
- ▶ If all FF change state together \Rightarrow *synchronous counter*



Similarly, the *NOR* gate is also represented.

$$X = (x_0, x_1, \dots, x_{m-1}),$$

$$Y = (y_0, y_1, \dots, y_{m-1}) \text{ are}$$

(say) binary words.

$$\therefore, z = f(X, Y),$$


$$\text{if } z_i = f(x_i, y_i) \text{ for } i = 0, \dots, m-1.$$

$$\therefore, Z = \overline{XY} \Rightarrow (z_0, z_1, \dots, z_{m-1})$$

$$= (\overline{x_0 y_0}, \overline{x_1 y_1}, \dots, \overline{x_{m-1} y_{m-1}}).$$

Figure 6: m-bit NAND word gate.

Serial addition

 

- ▶ Two-bit addition takes place for each clock pulse. $z(t) = x(t) + y(t)$.
- ▶ It may produce a carry bit $c(t)$. Thus two states (S_0, S_1) are possible, for $c(t-1) = 0$, and $c(t-1) = 1$. Thus, $z(t) = x(t) + y(t) + c(t-1)$.

state	input x_1x_2			
	00	01	10	11
s_0	$s_0, 0$	$s_0, 1$	$s_0, 1$	$s_1, 0$
s_1	$s_0, 1$	$s_1, 0$	$s_1, 0$	$s_1, 1$

- ▶ Each entry has form $s(t+1), z(t)$. y is FF's state variable, $y = 0$ for s_0 , and $y = 1$ for s_1 .

Logic circuit for Serial addition

 


Figure 7: Serial Adder

Word Level Design: Parallel addition

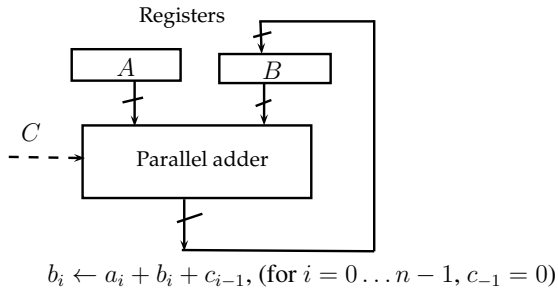


Figure 8: Word adder

K input m-bit multiplexer

- ▶ There are k input lines, each m -bit wide.
- ▶ The number of select lines p to select a unique input are given by expression $k = 2^p$, where total number of inputs are k .
- ▶ Source selection is determined by an *encoded* pattern of p -bits.
- ▶ $z_j = \sum_{i=0}^{k-1} x_{ij} a_i e$, for $j = 0, 1, \dots, m-1$

 


Figure 9: k-input m-bit multiplexer.

2 input 4-bit Multiplexer

2-input 4-bit word multiplexer

 


Figure 10: 2-1 multiplexer

- ▶ It has two input words, each 4-bit long (x_0, x_1, x_2, x_3 and y_0, y_1, y_2, y_3).
- ▶ Select line selects either $x_0x_1x_2x_3$ or $y_0y_1y_2y_3$, and delivers at o/p as $z_0z_1z_2z_3$.
- ▶ expression?

Decoders and Encoder

- ▶ **Decoder:** 1-out-of- 2^n or $1/2^n$ decoder is a combinational circuit with n input lines and 2^n o/p data lines.
- ▶ For input $x_0x_1=00, 01, 10, 11$ the output $z_0z_1z_2z_3$ is 1000, 0100, 0010, 0001 respectively. Hence 2- to-4 decoder.

 



Figure 11: 2-4 decoder

- ▶ **Encoder:** generates the address. It has inverse function of decoder. Has 2^k i/p lines and k output lines.

4-to-2 encoder


Simple Encoder: It is too much restricted. For the required outputs, the input should be exactly as shown. If input deviates from the given, the output is undecidable.

A_3	A_2	A_1	A_0	F_1	F_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

Priority Encoder: It generates the output corresponding to the bit it does for simple encoder. X indicates do'nt care bits.

A_3	A_2	A_1	A_0	F_1	F_0
0	0	0	0	x	x
0	0	0	1	0	0
0	0	1	x	0	1
0	1	x	x	1	0
1	x	x	x	1	1

 

1. Find a minimum cost implementation of the function $f(x_1, x_2, x_3, x_4)$, where $f = 1$ if either one or two of the input variables have the logic value 1. Otherwise, $f = 0$.
2. Prove that associative rule does not apply to the *NAND* operator.
3. How you will construct a down counter, i.e, from 1111 to 0000 ?
4. The address lines $A_0 \dots A_{15}$, use encoder to access the corresponding physical address (T/F).